

( 2 )

Code : 031201

B.Tech 2nd Semester Exam., 2018

BASIC ELECTRICAL ENGINEERING

Time : 3 hours


Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.  
 (ii) There are **NINE** questions in this paper.  
 (iii) Attempt **FIVE** questions in all.  
 (iv) Question No. 1 is compulsory.

1. Choose the correct answer of the following  
 (any seven) :  $2 \times 7 = 14$

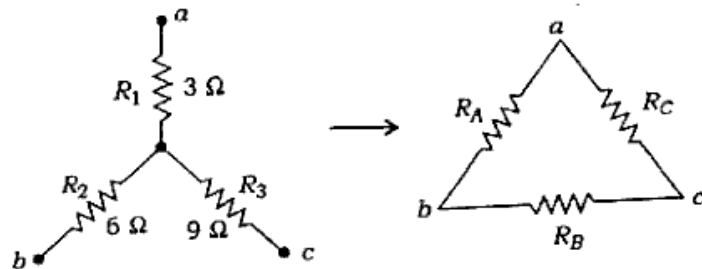(a) A star-connected network which is equivalent to the delta network is shown in the figure given below. The  $R_A$ ,  $R_B$  and  $R_C$  (in ohm) are respectively



- (i) 99  $\Omega$ , 33  $\Omega$ , 16.5  $\Omega$   
 (ii) 11  $\Omega$ , 16.5  $\Omega$ , 33  $\Omega$   
 (iii) 11  $\Omega$ , 33  $\Omega$ , 16.5  $\Omega$   
 (iv) 1  $\Omega$ , 3  $\Omega$ , 1.5  $\Omega$

( Turn Over )

(b) Superposition theorem is not applicable for

- (i) voltage calculation  
 (ii) bilateral elements  
 (iii) power calculation  
 (iv) passive elements

(c) Nodal analysis is based on

- (i) KCL  
 (ii) KVL  
 (iii) Both (i) and (ii)  
 (iv) law of conservation of energy

(d) The r.m.s. value of sine wave is 100 A. Its peak is

- (i) 70.7 A  
 (ii) 141 A  
 (iii) 150 A  
 (iv) 282.8 A

8AK/332

8AK/332

( Continued )

( 3 )

(e) A voltage is represented by a sine wave and has a maximum value of 100 V. Its r.m.s. and average value are respectively

- (i) 70.7 V, 63.6 V
- (ii) 0.707 V, 0.637 V
- (iii) 70.7 V, 0.63 V
- (iv) 0.707 V, 63.6 V

(f) An a.c. source of 200 V r.m.s. supplies active power of 600 W and reactive power of 800 VAR. The r.m.s. current drawn from the source is

- (i) 10 A
- (ii) 5 A
- (iii) 3.75 A
- (iv) 2.5 A

(g) The hysteresis and eddy current losses of a 1- $\phi$  transformer working on 200 V, 50 Hz supply are  $P_h$  and  $P_e$  respectively. The percentage decrease in these losses when operated at 160 V, 40 Hz supply are respectively


- (i) 32, 36
- (ii) 20, 36
- ~~(iii) 25, 50~~
- (iv) 40, 80

( Turn Over )

8AK/332

( 4 )

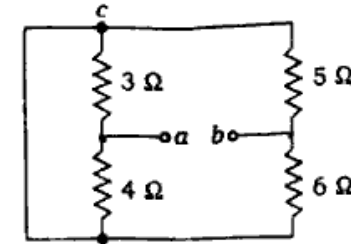(h) The resistance between the terminals  $a$ - $b$ , in the network shown in the figure given below, is



- (i) 4.44  $\Omega$
- (ii) 6.66  $\Omega$
- (iii) 7.77  $\Omega$
- (iv) 2.22  $\Omega$

(i) The average value of a sinusoidal waveform for complete cycle ( $v_{av}$ ) is

- (i)  $0.637 V_m$
- (ii)  $0.707 V_m$
- (iii) 0
- (iv) None of the above

(j) In a three-phase system, voltages differ in phase by


- (i)  $30^\circ$
- (ii)  $90^\circ$
- (iii)  $60^\circ$
- (iv)  $120^\circ$

8AK/332

( Continued )

( 5 )

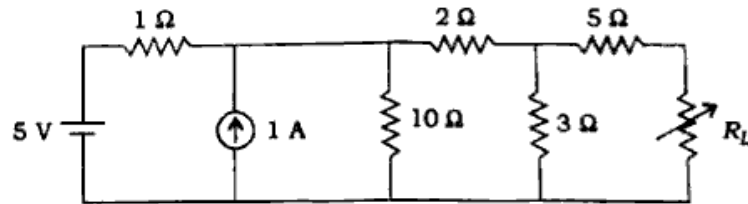2. (a) State and explain maximum power transfer theorem. 7
- (b) Find the value of resistance  $R_L$  in the figure given below for maximum power transfer and calculate maximum power : 7



3. (a) Define r.m.s. value and average value of sinusoidal waveform. 7
- (b) An RLC series circuit with a resistance of  $10\ \Omega$ , a inductance of  $0.2\ \text{H}$  and a capacitance of  $40\ \mu\text{F}$  is supplied with a  $100\ \text{V}$  supply at variable frequency. Find the following with respect to the series resonant circuit :
- Frequency of which resonance takes place
  - Current
  - Power
  - Power factor
  - Voltage across RLC at that time
  - Quality factor
  - Half-power points


8AK/332

( Turn Over )

( 6 )


4. (a) Define the following : 4
- Peak factor
  - Form factor

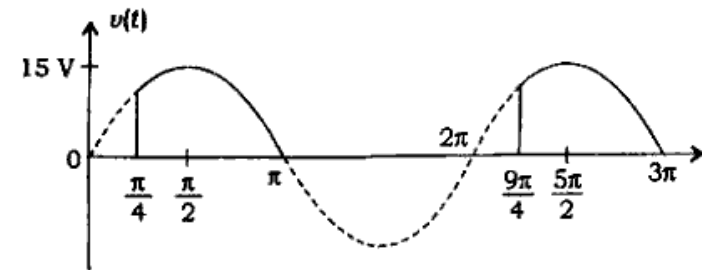- (b) The output voltage of an electronic device is given in the following figure :



- Determine (i) the average value and (ii) the r.m.s. value of the voltage. 10

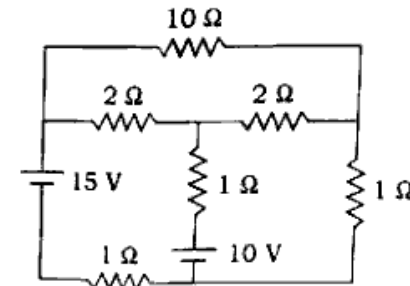5. (a) State and explain Thevenin's theorem. 7
- (b) Find the current through  $10\ \Omega$  resistor in the following figure by Thevenin's theorem : 7




8AK/332

( Continued )

( 7 )

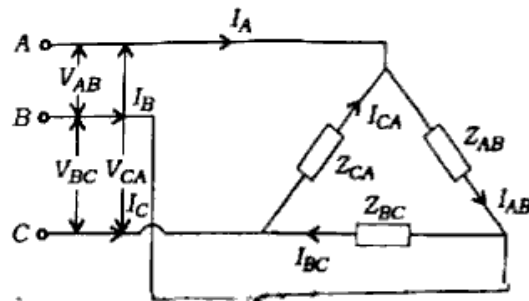6. In the circuit of figure given below, a 400 V, 50 Hz, 3-phase supply of phase sequence ABC is supplied to a delta-connected load consisting a  $100 \Omega$  resistor between lines A and B, a  $378 \text{ mH}$  inductor between lines B and C, and a  $37.8 \mu\text{F}$  capacitor between lines C and A. Determine phase and line currents. 14



7. (a) Explain B-H curve with neat diagram. 7  
 (b) A coil of 200 turns is wound uniformly over a wooden rim having a mean circumference of 60 cm and uniform cross-sectional area of  $5 \text{ cm}^2$ . If the current through the coil is 4 A, calculate (i) the magnetomotive force, (ii) the total flux and (iii) the flux density. 7
8. (a) What are the different types of moving-coil instrument? Explain any one in detail. 7

( Turn Over )

( 8 )

- (b) What are the different types of controlling torque? Explain any one in detail. 7
9. Write short notes on any two of the following : 7×2=14  
 (a) Star-delta conversion  
 (b) Superposition theorem  
 (c) Moving-iron instruments

\*\*\*